

## Solution for PHYCS 102 Test II dated 28/11/2000

$$\left. \begin{aligned} Q_1 + Q_2 &= 150 \mu \\ V &= \frac{Q_1}{10 \mu} = \frac{Q_2}{5 \mu} \end{aligned} \right\} \begin{aligned} Q_1 &= 100 \mu c \\ Q_2 &= 50 \mu c \end{aligned}$$

1.

2. The upper loop:

$$2I_1 + 5I_2 = 16 \quad \therefore I_1 = 3A$$

$$I_3 = I_1 - I_2 = 1A$$


The lower loop:

$$-2I_3 + 5I_2 = \varepsilon \quad \therefore \varepsilon = 8V$$

$$V_{ab} = 2I_1 + 3I_2 = 12V$$

**or**

$$V_{ab} = -2I_2 + 16 = 12V$$

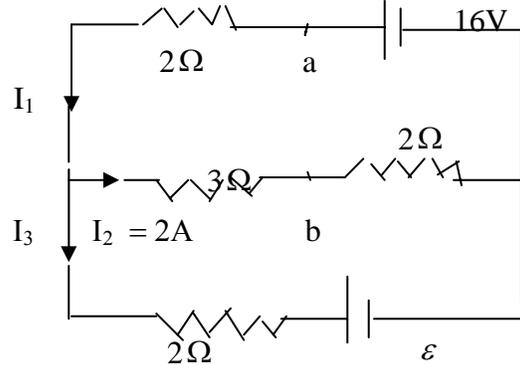

3a.  $C_1 = \frac{\varepsilon_0 A k}{d} = 15.93 \text{ PF}$ ,  $C_2 = \frac{\varepsilon_0 A}{d} = 8.85 \text{ PF}$   
 $C = C_1 + C_2 = 24.78 \text{ PF}$

b.  $E_1 = \frac{V}{kd} = 5.56 \times 10^4 \text{ V/m}$

4a.  $C_{eq} = \{C_1 = (C_2 // C_3)\}$ ,  $C_{eq} = \frac{30(10+5)}{30+(10+5)} = 10 \mu F$

b.  $V_1 = \frac{Q_1}{C_1} = \frac{C_{eq} \times 60}{C_1} = 20V$

**or**

$$\left. \begin{aligned} 60 &= V_1 + V_2 \\ Q &= 30V_1 = 15V_2 \end{aligned} \right\} \Rightarrow V_1 = 20V$$

5a.  $P = \frac{V^2}{R}$ ,  $R = 80.67 \Omega$

b.  $I = \frac{V}{R} = 2.73A$ ,  $J = \frac{I}{A} = 13.9 \times 10^6 \text{ A/m}^2$

c.  $E = \rho J = 0.778 \text{ V/m}$

d.  $n = D N_{av} / A = 6.29 \times 10^{22} / \text{cm}^3$

$$J = nev_d, \quad v_d = 1.38 \text{ mm/s}$$