

University of Bahrain  
College of Science  
Department of Physics

# PHYCS 102

## Test (II)

Time: 11:00 – 11:50 am

Date: 22<sup>nd</sup> May 2001

Name:-----ID#-----Sec:-----  
---

Qts	Marks	100
1		
2		
3		
4		
<b>Total</b>	<b>100</b>	

**Important data:**

$$e^- = e^+ = 1.6 \times 10^{-19} \text{C}$$


$$m_e = 9.1 \times 10^{-31} \text{kg}$$

$$m_p = 1.67 \times 10^{-27} \text{kg}$$

$$k = \frac{1}{4\pi \epsilon_0} = 9 \times 10^9 \frac{\text{Nm}^2}{\text{C}^2}$$

$$g = 10 \text{ m/s}^2$$

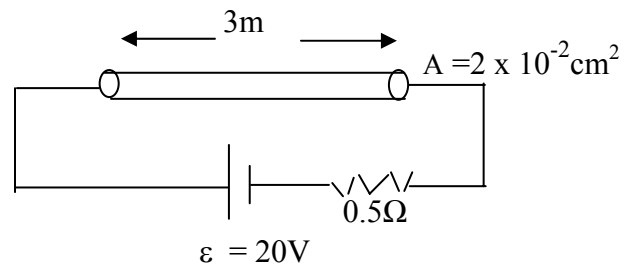1. A tungsten wire of length 3m and cross section area of  $2 \times 10^{-2} \text{cm}^2$  is connected with a source of emf = 20V, and internal resistance of  $0.5\Omega$ , find:
- The resistance of the wire assuming ( $\rho = 5.6 \mu \Omega \cdot \text{cm}$ )
  - The current density in the tungsten wire.
  - The electric field in the wire.
  - The electron drift velocity. The concentration of electrons in the tungsten wire is  $n = 6.32 \times 10^{22}/\text{cm}^3$ .



$$\text{a) } R = \frac{\rho \ell}{A} = \frac{(5.6 \times 10^{-8})(3)}{2 \times 10^{-6}} = 8.4 \times 10^{-2} \Omega$$

$$\text{b) } I = \frac{\varepsilon}{R + r} = 34.24 \text{ A}$$

$$J = \frac{I}{A} = 1.712 \times 10^7 \text{ A/m}^2$$


$$\text{c) } E = \rho J = 0.958 \text{ V/m}$$

$$\text{/or/ } \left. \begin{array}{l} 20 = V_R + V_r \\ \frac{V_R}{8.4 \times 10^{-2}} = \frac{V_r}{0.5} \end{array} \right\} \begin{array}{l} V_R = 2.876 \text{ V} \\ E = \frac{V_r}{L} = 0.958 \text{ V/m} \end{array}$$

$$\text{d) } J = ne v_d, \quad v_d = 1.69 \times 10^{-3} \text{ m/s}$$

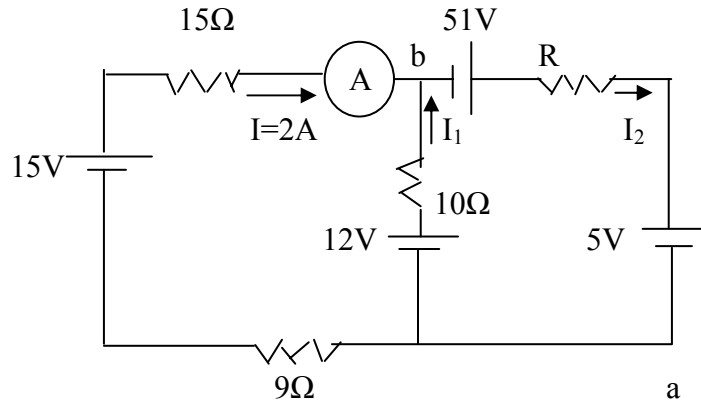**Q2.** The ammeter reads 2A, find the following:

- $I_1$ ,  $I_2$  and  $R$ .
- The power dissipated in the  $10\Omega$  resistor.
- The potential difference  $V_{ab}$ .



$$\mathbf{a)} \quad V_{ab} = \sum_K I_K R_K - \sum_K \varepsilon_K = (9+15)(2) - 15 = 33V$$

$$\therefore 33 = 10I_1 - 12 \quad \therefore I_1 = 4.5A \text{ and } I_2 = 6.5A$$

$$\text{/or/loop: } 15 \times 2 - 10I_1 + 9 \times 2 = -12 + 15 \Rightarrow I_1 = 4.5A$$

$$R : 33 = (-6.5)R - (5 - 51) \Rightarrow R = 2\Omega$$

$$\text{/or/ } (6.5)R + (4.5)10 = -5 + 12 + 51 \Rightarrow R = 2\Omega$$


$$\mathbf{b)} \quad P = I_1^2 R = (4.5)^2 (10) = 202.5 W$$

$$\mathbf{c)} \quad V_{ab} = 33V$$

**Q3.** Consider the circuit shown below. Calculate, after a long time of connection, the

- a. Voltage  $V_{ab}$
- b. Charge of the capacitor.

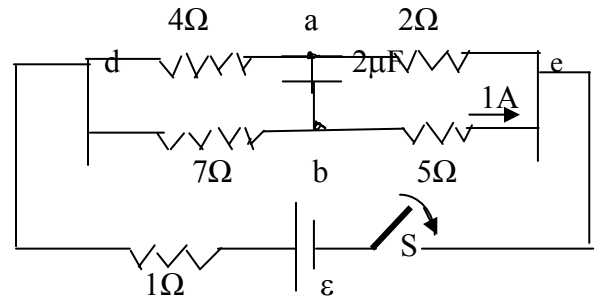c. If the switch (s) is opened, how long does it take for the capacitor to discharge to  $\left(\frac{1}{5}\right)$  of its initial charge?



a)  $V_{de} = (7 + 5) \times 1 = 12V$  ,  $12 = 6I_2 \Rightarrow I_2 = 2A$

$V_{ab} = V_{ad} + V_{db} = (-2)(4) + (1)(7) = -1V$


$\therefore V_{ba} = 1V$

b)  $q_0 = CV_c = 2 \mu C$

c)  $q = q_0 e^{-t/\tau}$

$\frac{1}{5} = e^{-t/\tau}$


$t = \tau - \ln 5 = 13.77 \mu s$

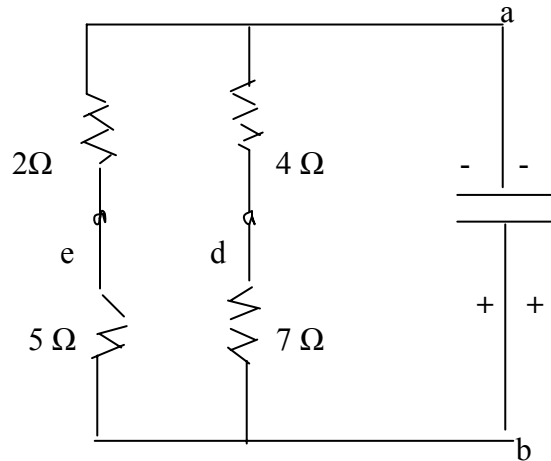

$R = \frac{(11)(7)}{11+7} = 4.28\Omega$

$\tau = RC = 8.56 \mu S$

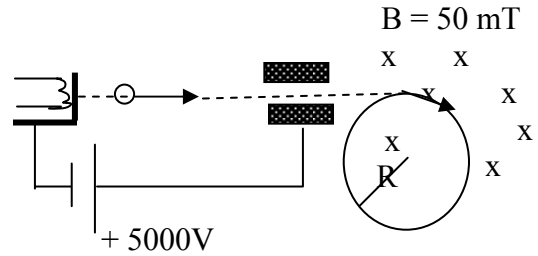4. The accelerating voltage that is applied to an electron beam is 5000V. The beam enters a region of uniform magnetic field of 50 mT perpendicular to the page as shown. Determine:
- The velocity of electrons in the beam.
  - The radius of the electron trajectory.
  - Draw the path of the electron in the region of the external magnetic field.



a) 
$$eV = \frac{1}{2}mv^2$$

$$v = 4.193 \times 10^7 \text{ m/s}$$

b) 
$$R = \frac{mv}{eB} \Rightarrow R = 0.47 \text{ cm}$$