

Name: _____ ID no.: _____

$$k = 9 \times 10^9 \text{ Nm}^2/\text{C}^2,$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2$$


$$e = 1.6 \times 10^{-19} \text{ C},$$

$$m_e = 9.11 \times 10^{-31} \text{ Kg},$$

$$m_p = 1.67 \times 10^{-27} \text{ Kg},$$

$$g = 10 \text{ m/s}^2$$

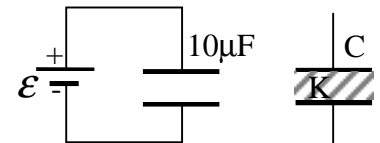Q1: An air filled capacitor of $C_0 = 10\mu\text{F}$ is fully charged using a 12 V battery as shown in the figure. The capacitor is then disconnected from the battery and filled with a dielectric material of $K= 4$. The electric potential (in V) across the capacitor after being filled with the dielectric is:




- (A) 2 (B) 3 (C) 4 (D) 5 (E) 6


Q2: The density of free electrons in gold is $5.9 \times 10^{28} \text{ m}^{-3}$. A gold wire, 10mm in diameter and carries a current of 5 A. The drift velocity (in $\mu\text{m/s}$) of the electrons in the wire is:

- (A) 2.7 (B) 4 (C) 5.4 (D) 6.7 (E) 8.1

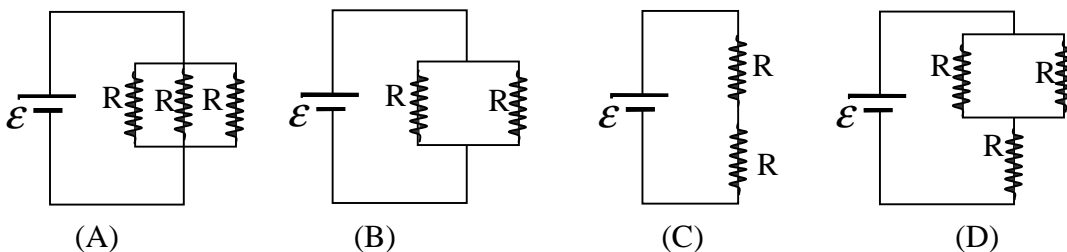Q3: In the circuits shown, all batteries have the same emf (\mathcal{E}) and all resistors are equal. In which circuit is the power supplied by the battery greatest?




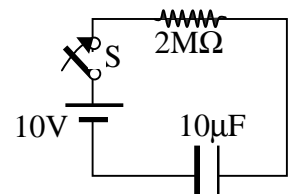Q4: In the circuit shown, the capacitor is initially uncharged. The switch S is closed at time $t=0$. When the charge on the capacitor is $52.76 \mu\text{C}$ the current (in μA) in the circuit is:



- (A) 3.89 (B) 3.03 (C) 2.36 (D) 1.84 (E) 1.43

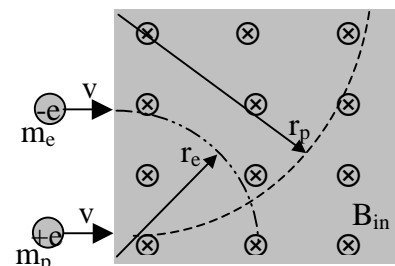Q5: A proton and electron have the same speed (v) and enter a region of uniform magnetic field pointing into the plane of the page as shown in the figure. If the radius of the electron's path $r_e = 0.5 \text{ cm}$ then the radius of the proton's path r_p (in cm) is:
(Note: $m_p/m_e = 1833$)



- (A) 183.3 (B) 366.6 (C) 550 (D) 733.2 (E) 916.5

Solutions of the above questions


Q1: $Q_i = Q_f \rightarrow C_o \times 12 = 4C_o \times V \therefore V = 3V$

Q2: $I = An_e e v_d, \quad v_d = 6.7 \mu m / s$

Q3: $P_{\text{supplied}} = P_{\text{dissipated}} = \mathcal{E} I = \frac{\mathcal{E}^2}{R_{\text{eq}}}$, greatest (P) corresponds to lowest R_{eq} , as in Fig(A)

Q4: $Q = C\mathcal{E}(1 - e^{-t/\tau})$ and $I = \frac{\mathcal{E}}{R} e^{-t/\tau}$, then $I = \frac{\mathcal{E}}{R} \left(1 - \frac{Q}{C\mathcal{E}}\right) = 2.36 \mu A$

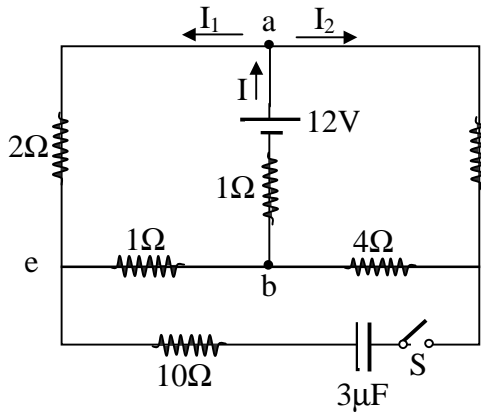Q5:
$$\left. \begin{array}{l} r_e = \frac{m_e v_e}{eB} \\ r_p = \frac{m_p v_p}{eB} \end{array} \right\} \frac{r_e}{r_p} = \frac{m_e}{m_p}, r_p = 1833 r_e = 916.5 cm$$



Problem (1) (30 Marks):
 For the circuit shown the switch S is open and the capacitor is uncharged. Find:
 (a)- The current I.

$$\left. \begin{array}{l} \text{Left loop 1: } 12 = I + 3I_1 \\ \text{Right loop 2: } 12 = I + 6I_2 \end{array} \right\} I_1 = 2I_2$$

$$12 = (I_1 + I_2) + 3I_1, \quad I_2 = \frac{12}{9} \text{ A}, I_1 = \frac{24}{9} \text{ A}$$

$$\therefore I = 4 \text{ A}$$

(b) The power supplied by the battery.

$$P_s = \varepsilon I = 48 \text{ W}$$

(c)- The magnitude of the potential difference between points a and b (V_{ab}).

$$V_{ab} = \sum_k I_k R_k - \sum_k \varepsilon_k = (-I) \times 1 - (-12) = 8 \text{ V}$$


or $V_{ab} = (I_1)(3) = 8 \text{ V}$

Now the switch S is closed for a long time.

(d)- What will be the current in the 10Ω resistor?

C is fully charged

$$I_C = \text{Zero}$$

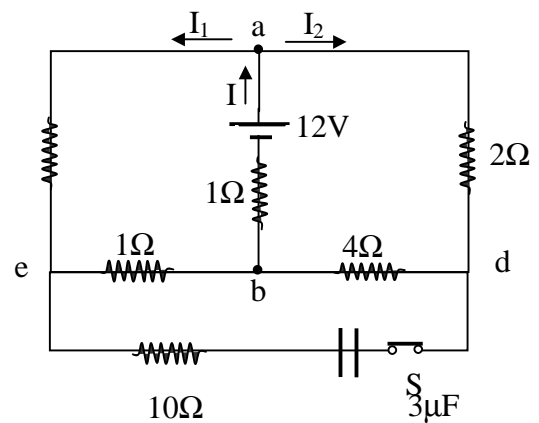

(e)- Find the charge on the capacitor.

$$V_c = V_{de} = (I_2)(4) + (-I_1)(1)$$


$$= 2.667 \text{ V}$$

$$Q = CV_c = 8 \mu\text{C}$$

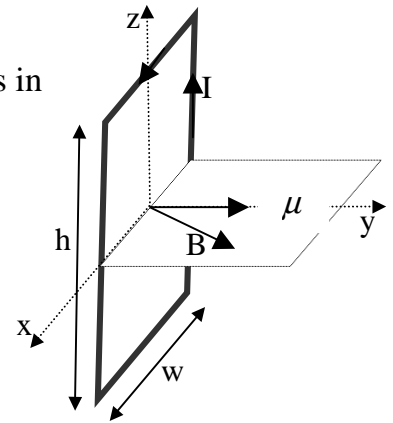Problem (2) (20 Marks):

A rectangular loop of height $h = 0.6$ m and width $w = 0.2$ m lies in the x - z plane as shown in the figure. If the loop carries a current of $I = 20$ A and is placed in a uniform magnetic field.

$\vec{B} = 0.3\hat{i} + 0.4\hat{j}$ (T) (i.e. B lies in the x - y plane) then find:



- (a)- The **magnitude and direction** of the magnetic dipole moment (μ) of the loop.

$$|\vec{\mu}| = IA = 2.4 \text{ A.m}^2$$

$$\vec{\mu} = 2.4 \vec{j} \text{ (A.m}^2\text{)}$$

- (b)- The initial **magnitude and direction** of the torque on the loop.

$$\vec{\tau} = \vec{\mu} \wedge \vec{B} = 2.4 \vec{j} \wedge [0.3 \vec{i} + 0.4 \vec{j}]$$

$$\vec{\tau} = 0.72 \left(-\vec{k} \right) \text{ N.m}$$

$$\text{magnitude} = 0.72 \text{ N.m}$$

$$\text{direction} = -\vec{k}$$