

Name:-----ID no.-----Sec.no.-----


Use: $g = 10 \text{ m/s}^2$, $\epsilon_o = 8.85 \times 10^{-12} \text{ C}^2 / \text{N.m}^2$, $K = 9 \times 10^9 \text{ N.m}^2/\text{C}^2$

- 1) A parallel-plate capacitor of plate separation $d = 1.0 \text{ mm}$ is filled with an insulator of dielectric constant $k = 2.5$ (3.0, 3.5, 4.0). The capacitor is charged to a potential difference of 10V. Find the charge density σ of the capacitor (in nC/m^2).

- a) 221.2 b) 265.5 c) 309.7 d) 354.0

Ans: $Q = CV \therefore \sigma = \frac{\epsilon_o k V}{d} = 221.2$

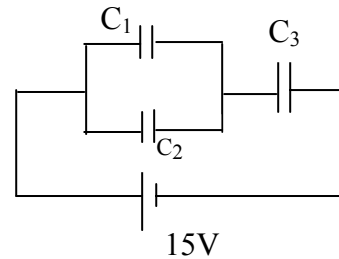
- 2) Three capacitors are connected as shown in the figure where $C_1 = 0.25 \mu\text{F}$, $C_2 = 0.75 \mu\text{F}$ and $C_3 = (1.0, 2.0, 3.0, 4.0) \mu\text{F}$. Find the charge (in μC) on the capacitor C_3 .



- a) 7.5 b) 10.0 c) 11.3 d) 12.0


Ans: $C_{eq} = \{(C_1 // C_2) = C_3\} = \frac{1 \times 1}{1+1} = 0.5 \mu\text{F}$; $Q = Q_3 = C_{eq} \times 15 = 7.5 \mu\text{C}$

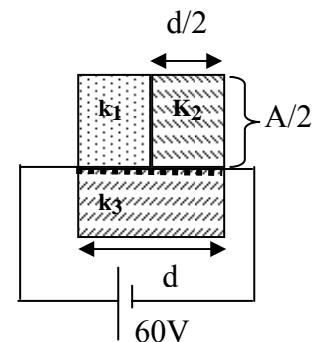- 3) A parallel-plate capacitor of plate area $A = 10 \text{ cm}^2$ and plate separation $d = 2 \text{ mm}$ is constructed using three insulators of $k_1 = 2.5$ (3.5, 4.5, 6.5), $k_2 = 5.0$ and $k_3 = 6.2$, as shown in the figure. Find the voltage across the dielectric of constant k_1 .



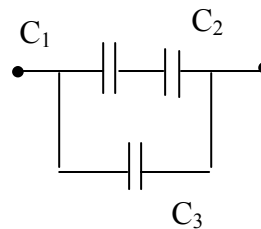
- a) 40.0 b) 35.3 c) 31.6 d) 26.0

Ans: $C_1 = \frac{\epsilon_o k_1 \left(\frac{A}{2}\right)}{(d/2)} = 11.06$, $C_2 = 22.12$
 $V_1 + V_2 = 60$; $C_1 V_1 = C_2 V_2$
 $\therefore V_1 = 40\text{V}$



- 4) Starting from the uncharged state of the shown circuit, the time (in s) that it takes for the charge to reach the value 2.5 (3.3, 3.0, 2.0) $\times 10^{-5}C$ is :

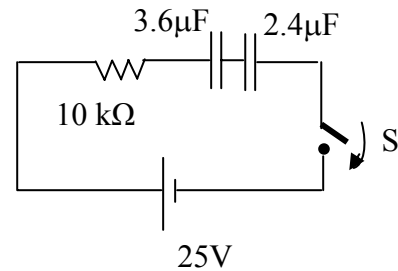- a) 1.71×10^{-2} b) 3.58×10^{-2}
 c) 2.58×10^{-2} d) 1.17×10^{-2}




Ans: $C_{eq} = \frac{3.6 \times 2.4}{3.6 + 2.4} = 1.44 \mu F$, $\tau = RC = 1.44 \times 10^{-2} s$,

$Q_o = C_{eq} \varepsilon = 36 \mu C$, $Q = Q_o (1 - e^{-t/\tau})$

$t = -\tau \ln \left(1 - \frac{Q}{Q_o} \right) = 1.71 \times 10^{-2} s$

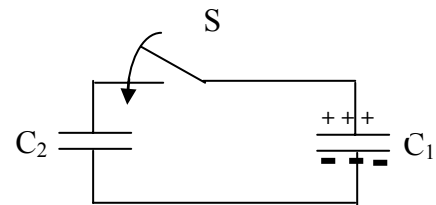- 5) The capacitor $C_1 = 3 \mu F$ that was fully charged to a potential difference of 10V is now connected to another uncharged capacitor $C_2 = 1.5$ (1.0, 0.75, 0.6) μF by closing of the switch S as shown in the figure. Find the final charge of C_2 (in μC).



- a) 10.0 b) 7.5 c) 6.0 d) 5.0

Ans:
$$\left. \begin{aligned} Q_o = C_1 V = 30 \mu C \text{ , } 30 \mu = Q_1 + Q_2 \\ \frac{Q_1}{C_1} = \frac{Q_2}{C_2} \end{aligned} \right\} \begin{aligned} Q_1 &= 2Q_2 \\ Q_2 &= 10 \mu C \end{aligned}$$

- 6) A battery with an electromotive force $\varepsilon = (6, 7, 8, 9)V$ and internal resistance of 0.5Ω is connected to 4.5Ω resistor. The power (in Watt) consumed by the resistor has a value of:-

- a) 6.48 b) 8.82 c) 11.52 d) 14.58

Ans: $P = I^2 R = \left(\frac{\varepsilon}{R+r} \right)^2 R = 6.48 W$

- 7) Nicrome wire of radius 0.32 mm, length 1m, and resistivity $150 \mu \Omega \cdot cm$. If the electric power dissipated in the wire is 73.6 (95.4, 120.3, 150.7)W, find the electric field in (V/m) inside the wire.

- a) 18.5 b) 21.1 c) 23.7 d) 26.5

Ans: $R = \frac{\rho \ell}{A} = 4.66 \Omega$, $\rho = \frac{V^2}{R} = \frac{E^2 \ell^2}{R}$, $E = \frac{\sqrt{PR}}{\ell} = 18.5 V/m$


8) A certain light bulb has a tungsten filament with a resistance of 19.0Ω when cold (20°C) and of $(140, 120, 90, 70) \Omega$ when hot. Find the temperature ($^\circ\text{C}$) of the filament when hot. (the temperature coefficient of resistivity α is $4.5 \times 10^{-3} \text{ }^\circ\text{C}^{-1}$).

- a) 1.44×10^3 b) 1.20×10^3 c) 850.4 d) 616.5

Ans: $R_h = R_c [1 + \alpha(T - 20)]$, $T = \frac{R_h - R_c}{\alpha R_c} + 20 = 1435.2^\circ\text{C}$

9) In the shown circuit, if $\epsilon_1 = 21$ (18,15,12)V and $\epsilon_2 = 11$ (8,5,2) V, then ϵ (in volt) is:


- a) 12 b) 9 c) 6 d) 3

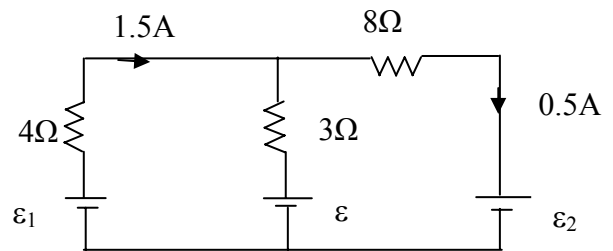

Ans: $V_{ab} = -1.5 \times 4 + 21 = 15\text{V}$, $15 = +1 \times 3 + \epsilon$, $\epsilon = 12\text{V}$

10) In the shown circuit, $\epsilon_1 = 9$ (8,6,5)V and $\epsilon_2 = 12\text{V}$. The potential difference V_{ab} across the resistance 6Ω (in volts) is:

- a) 9.0 b) 8.73 c) 8.18 d) 7.90

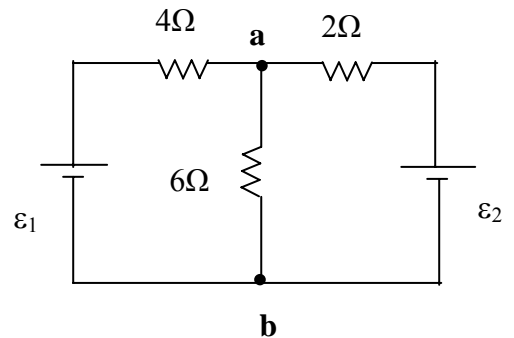

Ans:
$$\left. \begin{aligned} I_1 &= I_2 + I_3 \\ 4I_2 - 6I_3 &= -9 \\ 2I_1 + 6I_3 &= 12 \end{aligned} \right\} \Rightarrow I_3 = 1.5\text{A}, V_{ab} = 1.5 \times 6 = 9\text{V}$$

