University of Bahrain College of Science Department of Physics

PHYCS 102 Test (II)

Time: 11:00 – 11:50 am

Date: 22nd May 2001

Name:	ID#	Sec:

Qts	Marks	
1		
2		
3		100
4		100
Total	100	


Important data:

$$e^{-}=e^{+}=1.6 \times 10^{-19} \text{C}$$
 $m_{\rm e}=9.1 \times 10^{-31} \text{ kg}$
$$m_{\rm p}=1.67 \times 10^{-27} \text{kg}$$


$$k=\frac{1}{4\pi \varepsilon_o}=9 \times 10^{9} \frac{Nm^2}{C^2}$$

$$g=10 \text{ m/s}^2$$

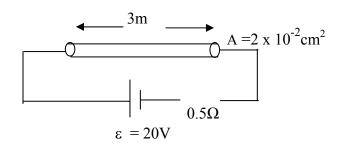
- 1. A tungsten wire of length 3m and cross section area of $2 \times 10^{-2} \text{cm}^2$ is connected with a source of emf = 20V, and internal resistance of 0.5Ω , find:
 - a. The resistance of the wire assuming ($\rho = 5.6 \mu \Omega$. cm)
 - **b.** The current density in the tungsten wire.
 - **c.** The electric field in the wire.
 - **d.** The electron drift velocity. The concentration of electrons in the tungsten wire is $n = 6.32 \times 10^{22} / \text{cm}^3$.



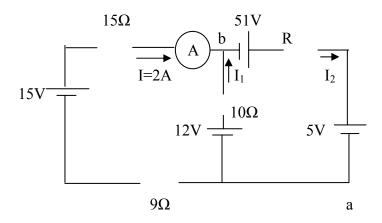- **Q2.** The ammeter reads 2A, find the following:
 - **a.** I_1 , I_2 and R.
 - **b.** The power dissipated in the 10Ω resistor. **c.** The potential difference V_{ab} .



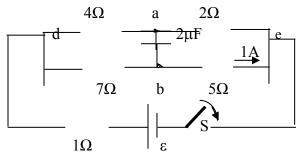- Q3. Consider the circuit shown below. Calculate, after a long time of connection, the
 - \mathbf{a} . Voltage V_{ab}
 - **b.** Charge of the capacitor.
 - c. If the switch (s) is opened, how long does it take for the capacitor to discharge to $(\frac{1}{5})$ of its initial charge?



- **4.** The accelerating voltage that is applied to an electron beam is 5000V. The beam enters a region of uniform magnetic field of 50 mT perpendicular to the page as shown. Determine:
 - **a.** The velocity of electrons in the beam.
 - **b.** The radius of the electron trajectory.
 - **c.** Draw the path of the electron in the region of the external magnetic field.

